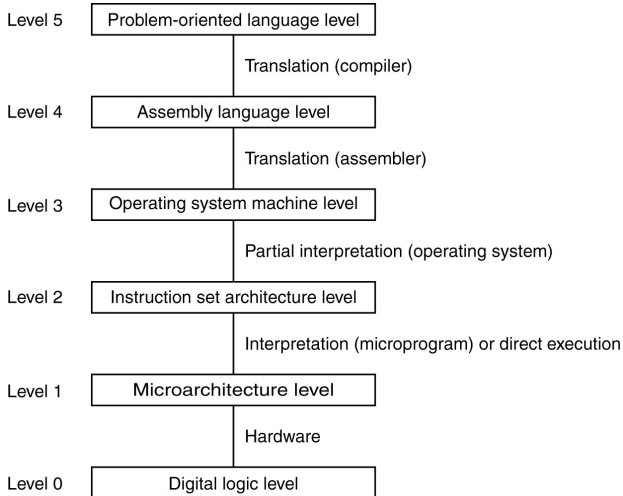


# Boolean Algebra, Gates and Circuits

Kasper Brink  
November 14, 2018

(Images taken from Tanenbaum, Structured Computer Organization,  
Fifth Edition, (c) 2006 Pearson Education, Inc.)

# Multi-level Architecture



# Analog vs. Digital Logic

Digital computers process *discrete* information.

All information is represented by two logical values:

logic 0 → e.g. voltage between 0.0 and 0.5 V

logic 1 → e.g. voltage between 1.0 and 1.5 V

To design and analyze digital circuits we make use of *Boolean Algebra*.

# Boolean Values and Operators

Boolean values  $B = \{0, 1\}$

Boolean variables  $x \in B$

Boolean operator		corresponds to Logic operator	
$\bar{x}$	complement (NOT)	$\neg p$	negation
$x \cdot y$	product (AND)	$p \wedge q$	conjunction
$x + y$	sum (OR)	$p \vee q$	disjunction

$x$	$\bar{x}$
0	1
1	0

$x$	$y$	$xy$
0	0	0
0	1	0
1	0	0
1	1	1

$x$	$y$	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

## Derived Operators

$\overline{xy}$     NAND

$\overline{x+y}$     NOR

$x \oplus y$     XOR (exclusive or)

$x$	$y$	$\overline{xy}$	$\overline{x+y}$	$x \oplus y$
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	0	0

## Boolean Functions

Boolean function of degree  $n$ :  $f : B^n \rightarrow B$

We can describe each Boolean function by its *truth table*, for example this function  $f : B^3 \rightarrow B$

$x$	$y$	$z$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

The function  $f$  is true iff exactly one of its arguments is true.

How many distinct Boolean functions of degree  $n$  exist?

$$2^{2^n}$$

## Boolean Expressions

Boolean expression: expression using 0, 1, boolean variables and operators.

Every Boolean expression represents a Boolean function.

Example:  $f(x, y) = x + \bar{y}$

$x$	$y$	$f(x, y)$
0	0	1
0	1	0
1	0	1
1	1	1

Conversely: can every Boolean function be written as a Boolean expression?

## Deriving a Boolean Expression for a Function

Example:

x	y	$f(x, y)$	
0	0	1	$\bar{x}\bar{y}$
0	1	0	
1	0	1	$x\bar{y}$
1	1	1	$xy$

This gives us  $f(x, y) = \bar{x}\bar{y} + x\bar{y} + xy$

Literal:  $x_i$  or  $\bar{x}_i$

Minterm: product of literals where each variable occurs exactly once

Expression for  $f$ : sum of the minterms where  $f = 1$

This is called the (*full*) *Disjunctive Normal Form* (DNF), or the “*sum of products*” representation.



## Equivalence of Boolean Expressions

Two Boolean expressions that represent the same Boolean function are called *equivalent*.

Example:  $x + \bar{y} = \bar{x}\bar{y} + x\bar{y} + xy$

You can prove this by showing that both expressions have the same truth table.

Often more convenient: rewriting expressions using the laws of Boolean algebra.

## Laws of Boolean Algebra

Name	Multiplicative form	Additive form
Complement	$\overline{\overline{x}} = x$	
Identity	$x \cdot 1 = x$	$x + 0 = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$
Idempotent	$x x = x$	$x + x = x$
Inverse	$x \bar{x} = 0$	$x + \bar{x} = 1$
Commutative	$xy = yx$	$x + y = y + x$
Associative	$x(yz) = (xy)z$	$x + (y + z) = (x + y) + z$
Distributive	$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$
Absorption	$x(x + y) = x$	$x + xy = x$
De Morgan	$\overline{xy} = \bar{x} + \bar{y}$	$\overline{x + y} = \bar{x} \bar{y}$

See also Tanenbaum, figure 3-6 (p. 156).

## Rewriting Expressions (1)

Example: rewrite the following expression to (full) DNF.

$$\begin{aligned}(x + z)(\overline{x + y}) &= (x + z)(\bar{x} \cdot \bar{y}) && \text{(de Morgan)} \\ &= x\bar{x}y + z\bar{x}y && \text{(distributivity, double complement)} \\ &= 0 + z\bar{x}y && \text{(inverse, null)} \\ &= \bar{x}yz && \text{(identity, commutativity)}\end{aligned}$$

## Rewriting Expressions (2)

Example: derive an expression for the following function, and simplify this.

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$\begin{aligned}f(x, y, z) &= \bar{x}y\bar{z} + x\bar{y}\bar{z} + xy\bar{z} && \text{(DNF)} \\&= (\bar{x}y + x\bar{y} + xy)\bar{z} && \text{(distributivity)} \\&= (\bar{x}y + x\bar{y} + (xy + xy))\bar{z} && \text{(idempotent)} \\&= (\bar{x}y + xy + x\bar{y} + xy)\bar{z} && \text{(commutativity)} \\&= ((\bar{x} + x)y + x(\bar{y} + y))\bar{z} && \text{(distributivity)} \\&= (y + x)\bar{z} && \text{(inverse \& null)} \\&= y\bar{z} + x\bar{z} && \text{(distributivity)}\end{aligned}$$

# Karnaugh Maps

*Karnaugh Map* is a graphical method for simplifying a Boolean expression.

Basic idea:

- Two minterms that differ in exactly one literal can be combined into a simpler term:

$$A\bar{B}CD + A\bar{B}\bar{C}D \longrightarrow A\bar{B}D$$

- Put all minterms in a table, ordered such that neighboring cells differ in exactly one literal.
- Visually locate blocks of minterms that can be combined, which are as large as possible.

## Karnaugh Maps: Example

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

		CD			
		00	01	11	10
AB	00	0	1	1	0
	01	0	1	1	0
	11	0	1	0	0
	10	1	1	0	1

$$F = \overline{A}D + \overline{C}D + A\overline{B}\overline{D}$$

## Karnaugh Maps: Rules

- Choose blocks to cover all the ones, but none of the zeros.
- Blocks are allowed to overlap.
- Blocks must:
  - be rectangular
  - have lengths of 1, 2 or 4
  - be as large as possible
- Use as few blocks as possible.
- Wrap around: top – bottom, left – right, corners

## Karnaugh Maps: Example 2

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

		BC			
		00	01	11	10
A	0	1	1	1	0
	1	1	1	0	1

$$F = \overline{B} + \overline{A}C + A\overline{C}$$



## Functional Completeness

- Every Boolean function can be expressed as a sum of products of literals (DNF).  
→ The set of operators  $\{\bar{\phantom{x}}, \cdot, +\}$  is *functionally complete*.
- The sets  $\{\bar{\phantom{x}}, \cdot\}$  and  $\{\bar{\phantom{x}}, +\}$  are also functionally complete.
- The operators NAND ( $\overline{xy}$ ) and NOR ( $\overline{x+y}$ ) are each functionally complete on their own.

# Gates en Circuits

# Digital Circuits

Physical implementation of digital logic:






Boolean values → signals in electronic circuit

Boolean operators → gates


Completeness: every Boolean function can be expressed with the help of a complete set of operators, for example  $\{\bar{\phantom{x}}, \cdot, +\}$  or  $\{\text{NAND}\}$ .

Therefore: every Boolean function can be implemented as a *circuit* by connecting gates from a complete set together!


# Gates

     


# How are Gates Implemented?

 

NOT-gate

 

NAND-gate

 


NOR-gate

# XOR


A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

$$A \oplus B = \bar{A}B + A\bar{B}$$

 


## Equivalence of Circuits

$AB + AC$

 

$A(B + C)$

 

# Combinational and Sequential Logic

## Combinational circuit

- output of circuit only depends on input (at the current time)
- implements a Boolean function
- acyclic circuit (mostly)


## Sequential circuit

- output of circuit depends on input *and* internal state
- implements a finite state machine
- cyclic circuit: feedback
- “circuit with memory”




# Majority

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

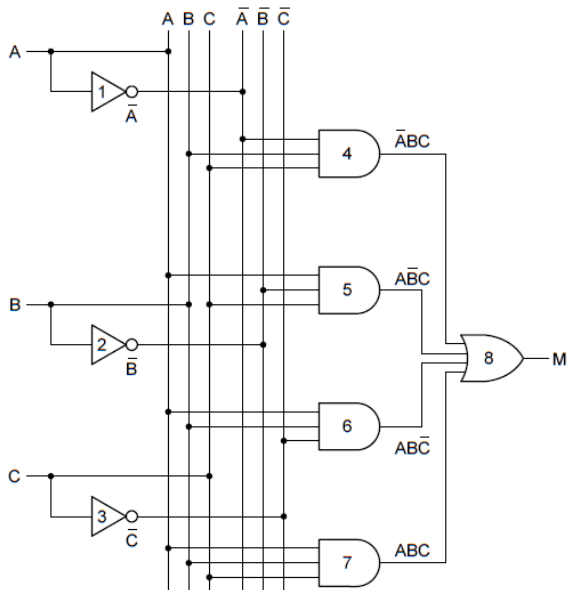


## Multiplexer: choose between signals

 

Circuit with data inputs  $D_0$  en  $D_1$  and control input  $S$ .  
If  $S = 0$ , the signal from  $D_0$  is passed to the output, else  $D_1$  is.


$$\text{Output } X = \bar{S} \cdot D_0 + S \cdot D_1$$

## Multiplexer with 8 inputs

 

 
# General Multiplexer

In general: a multiplexer with  $n$  control inputs selects one of the input signals  $D_0, \dots, D_{2^n-1}$  and passes this to the output.


 
## Decoder

The binary number on the  $n$  inputs determines which of the  $2^n$  outputs will become active (output a “1”).




## Half Adder

Adding two 1-bit numbers A en B:

A	0	1	0	1
B	0	0	1	1
	$\frac{00}{+}$	$\frac{01}{+}$	$\frac{01}{+}$	$\frac{10}{+}$

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = AB$$

 


## Full Adder

Adding 1-bit numbers with carry-in.

A	B	$C_{in}$	S	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$\text{Sum} = A \oplus B \oplus C_{in}$$
 
$$\text{Carry} = AB + (A \oplus B) \cdot C_{in}$$


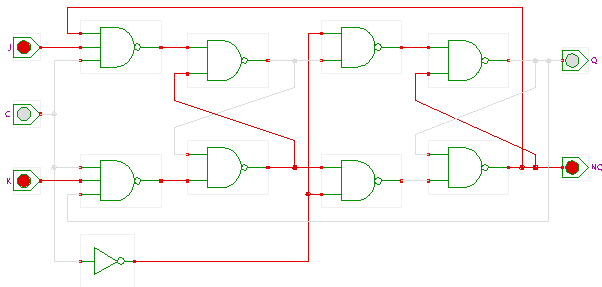
# Hades

- Practical assignment will be done in *Hades*, the *Hamburg Design System*.
- “Framework for interactive simulation”
- Can be downloaded from <https://tams.informatik.uni-hamburg.de/applets/hades/>





# Summary

## Boolean Algebra

- Boolean functions and expressions
- Disjunctive normal form
- Laws of Boolean algebra
- Karnaugh maps
- Functional completeness

## Gates and circuits

- Physical implementation of digital logic
- Combinational and sequential circuits
- Gate symbols
- Circuits: xor, majority, multiplexer, decoder, half adder, full adder.